

**EVN-2694**

Total Page No. : 2]

[Roll No. ....]

**BCA II Semester  
Examination, 2023-24**

**DIGITAL ELECTRONICS**

**Paper : IV**

**Time : 2 : 30 Hours]**

**[Max. Marks : 70**

**Note :** Attempt any *five* questions. All questions carry equal marks.

- Q. 1. (a) What are basic properties of Boolean algebra ?  
(b) Explain various number systems and codes and their conversion with example.
- Q. 2. (a) Explain the Karnaugh map with all its limitation.  
(b) What are called don't care condition ?
- Q. 3. (a) Draw the truth table for half adder circuit and Write the Boolean expression for sum and carry.  
(b) What is programmable logic array ?
- Q. 4. (a) Convert decimal 8723 to both BCD and ASCII Codes.  
(b) Simplify the following expression and draw truth table :

$$X \cdot Y + X (Y + Z) + Y (Y + Z)$$

( 1 )

P.T.O.

Q. 5. (a) Explain the following :

- (i) EEPROM
- (ii) Full adder
- (iii) Multiplexer
- (iv) JK flip-flop

(b) State the difference between the combinational and sequential circuit.

Q. 6. Implement the Boolean expression using :

$$f(A, B, C, D) = \Sigma(1, 2, 3, 4, 7, 9, 10, 12)$$

Q. 7. Do as directed :

- (a) Convert  $(67A9)_{16}$  into decimal
- (b) Add  $(+80)$  and  $(-70)$  using 2's complement
- (c) Difference between RAM and ROM
- (d) convert  $(657)_8$  into decimal
- (e) Explain different types of memory
- (f) Explain Universal gates
- (g) Define Decoders

\*\*\* <https://www.sdsuvonline.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से

**S-202**

**S-202**