

Z-175

Total Pages : 2

Roll No.

S-2452

B.C.A. (IInd Semester) Examination, 2021-22

DIGITAL ELECTRONICS

Paper-IV (BCA-204)

Time : 2:30 Hours]

Max. Marks : 70

Note : Attempt any *five* questions. All questions carry equal marks.

1. (a) Design and draw the logic diagram of full adder. [7]
(b) Explain the working of S-R flip-flop using its logic diagram and truth table. [7]
2. (a) What are universal gate? Explain NAND gate is a Universal gate. [7]
(b) Write short notes on EEPROM and EPROM. [7]
3. Perform the following number conversion : [2×7=14]
(a) $(3DEF)_{16} = (?)_{10}$
(b) $(F34A)_{16} = (?)_2$
(c) $(651)_8 = (?)_{10}$
(d) $(58)_{10} = (?)_2$

- (e) $(1100.1010)_2 = (?)_{16}$
- (f) $(7.56)_8 = (?)_{16}$
- (g) $(45.23)_{10} = (?)_2$

4. (a) Simplify the expression: [7]
 $F(A, B, C, D) = \Sigma (0, 2, 8, 9, 10, 11, 12, 14)$
Using K- Map in POS form and represent the resulting function using NOR gates.
(b) Construct a 4*16 decoder using two 3*8 decoders. [7]
5. (a) Explain the stack organization. Write the sequence of micro operation for PUSH and POP operation. [7]
(b) Explain the BCD, ASCII and EBCDIC. [7]
6. (a) Difference between cache memory and virtual memory. [7]
(b) Explain how a J-K flip flop can be converted into a D flip flop. <https://www.sdsuonline.com> [7]
7. Short notes (Any four) : [2×7=14]
(a) Hit Ratio and miss ratio.
(b) K-Map.
(c) Asynchronous data transfer.
(d) Multiplexer.
(e) Magnetic tape.

Z-175/S-2452

[P.T.O.]

Z-175/S-2452

[2]